

Lab 1: ALU with Arbiter

Submission Due Dates:

Demo: 2022/09/20 17:20

Source Code: 2022/09/20 18:30

Report: 2022/09/25 23:59

Objective

Getting familiar with basic Verilog behavior modeling.

Action Items

1 lab1_1.v (20%)

Write a Verilog module that models a **4-bit arbiter** and test your module using the testbench file **lab1_1_t.v**, Figure 1 is the block diagram of **lab1_1**.

 


Figure 1: lab1_1 block diagram

a. IO list:

✓ Input: **request[3:0]**

A 4-bit input vector: the *i*-th bit indicates the request from the *i*-th port, where *i*=0..3.

Example:

request	Description
4'b0101	Port 0 and port 2 have requests
4'b1000	Only port 3 has a request
4'b0000	No one has a request

✓ Output: **grant[3:0]**

A 4-bit one-hot vector outputs the grant based on following rule.

- If one port has a request, it will be granted (e.g., if the second port has a request, the **request** = 4'b0100. The **grant** should be 4'b0100 to grant this only request).
- If there are multiple requests, you should grant the port with the largest index. For example, if ports 0, 1, and 3 have requests at the same time, the **request** = 4'b1011. Then port 3 will be granted with the **grant** = 4'b1000.
- If there is no request, such that the **request** = 4'b0000, the **grant** should be

4'b0000.

Note: Please use Verilog *if-else* statement to implement this module, “case” or “casex” is not allowed

Example:

Input: request [3:0]	Output: grant [3:0]
4'b0101	4'b0100
4'b1000	4'b1000
4'b0000	4'b0000
4'b0011	4'b0010

b. You must use the following template for your design:

```
`timescale 1ns/100ps
module lab1_1 (
    input wire [3:0] request,
    output reg [3:0] grant
);
    /* Note that grant can be either reg or wire.
     * e.g.,    output reg [3:0] grant
     * or      output wire [3:0] grant
     * It depends on how you design your module. */
    // add your design here

endmodule
```

2 lab1_1_t.v (20%)

Complete the testbench **lab1_1_t.v** to verify your design. Check the TODO hints in the template code carefully. For incorrect results, you may see an error message like this:

Error: request = XXXX, grant = XX, correct grant should be XX
where X is the corresponding data bit.

3 lab1_2.v (30%)

Write a Verilog module that models a **4-bit Arithmetic Logic Unit (ALU)** and test your module using the testbench **lab1_2_t.v**. The **4-input arbiter, lab1_1**, must be reused to do the arbitration. Figure 2 is the block diagram of **lab1_2**.

 


Figure 2: lab1_2 block diagram

a. IO list:

- ✓ Inputs: **source_0[5:0]**, **source_1[5:0]**, **source_2[5:0]**, **source_3[5:0]**

Here are four 6-bit source ports **source_X**. The format of each port is listed below:

Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0
Control		Data			

- The **Control** of each source port indicates whether the port sends a request, and also the operation on its **Data**. The **Control** signal's function is listed below:

Control signal (Bit 5:4)	Function
2'b00	No request
2'b01	Request; masking with 4'b1010 result = Data AND 4'b1010
2'b10	Request; increment by 3 (ignoring the overflow) result = Data + 4'd3
2'b11	Request; local-left-shifting by two bits result = Data << 2

- ✓ Output: **result[3:0]**

A 4-bit vector to output the result, based on the following rules.

- There may be multiple source ports having requests at the same time, **but only the port with the greatest index will be granted**. To determine which port gets the grant, you must reuse the **lab1_1** module to do the arbitration and generate the **result**. E.g., if multiple source ports send their requests, only the granted port produces the **result** based on its **Control** and **Data**.

- If there is no request from **source_X**, set the **result** to 0.

Note: Please use Verilog “case” to implement this module, if-else statement is prohibited.

b. You must use the following template for your design:

```
`timescale 1ns/100ps
module lab1_2 (
    input wire [5:0] source_0,
    input wire [5:0] source_1,
    input wire [5:0] source_2,
    input wire [5:0] source_3,
    output reg [3:0] result
);
    /* Note that result can be either reg or wire.
     * It depends on how you design your module. */
    // add your design here
endmodule
```

c. Follow the **Appendix** to extend the simulation time and add the test patterns.

4 lab1_2_t.v (30%)

Complete the testbench **lab1_2_t.v** to verify your design. Check the TODO hints in the template code carefully. For incorrect results, you may see an error message like this:

**Error: source_0 = XX, source_1 = XX source_2 = XX, source_3 = XX
your result = XX, correct result = XX.**

where X are the corresponding data bits.

5 Questions and Discussion

Please answer the following questions in your report.

- In the testbench **lab1_1_t.v**, please explain why we place **#DELAY** between input assignment and output verification. Hint: Gate delay.
- In the testbench **lab1_1_t.v**, does the Verilog keyword **function** synthesizable? If yes, what kind of circuit will it be?
- Please explain the difference between **if-else** and **case** statements after the synthesis at the gate/cell-level. Hint: priority encoder.

6 Guidelines for the report

Your report should include but not limit to the following items.

Grading policy (subject to change): Part (A): 35%; Part (B): 50%; Part (C): 10%; (D): 5%

A. Lab Implementation

You may elaborate the followings.

1. Block diagram of the design with explanation
2. Partial code screenshot with the explanation: you don't need to paste the entire code into the report. Just explain the kernel part.
3. Event-based finite state machine (FSM) with the explanation:

Note1: Use events to describe the transition of FSM but not signals logic statement.

Note2: You don't need to do this part if there is no FSM in this lab.

B. Questions and Discussions

Provide your answer to the Questions and Discussions in the lab assignment.

C. Problem Encountered

Describe the problems you encountered, solutions you developed, and the discussion. Explaining them with code segments or diagrams is recommended.

D. Suggestions

Any suggestions for this course are more welcome.

(If not, you may also post a joke. A funny one, please. It is not mandatory and is nothing to do with the grading. But it would undoubtedly amuse us. ☺)


Attention

- ✓ **DO NOT** copy-and-paste code segments from the PDF materials. It may also paste invisible non-ASCII characters, leading to hard-to-debug syntax errors.
- ✓ You should hand in **four** source files, including **lab1_1.v**, **lab1_1_t.v**, **lab1_2.v**, **lab1_2_t.v**. **Upload each source file individually. DO NOT hand in any compressed ZIP files, which will be considered an incorrect format.**
- ✓ **lab1_2.v must** include the module of **lab1_1**. That is, you should copy lab1_1 into **lab1_2.v**. Otherwise, you will get a penalty of 20 points.
- ✓ We will use **hidden test patterns** to test your design in this lab.
- ✓ You should also hand in your report as **lab1_report_StudentID.pdf** (i.e., lab1_report_108456789.pdf).
- ✓ You should be able to answer questions of this lab from TA during the demo.
- ✓ You may also add a **\$monitor** in the testbench to show all the inputs and outputs during the simulation.


Appendix

- ✓ Before the simulation, you need to change the runtime to 10000ns (or a large enough period) in "Simulation Settings". See the guide below.

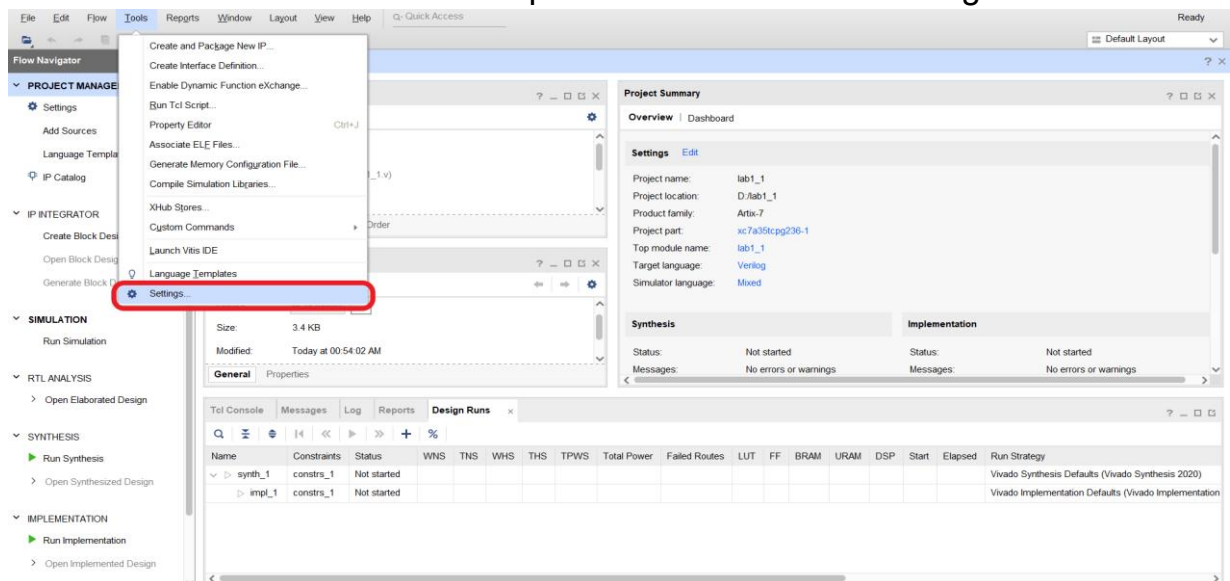
1. Click Tools at the top of Vivado and select settings.




2. Select Simulation.

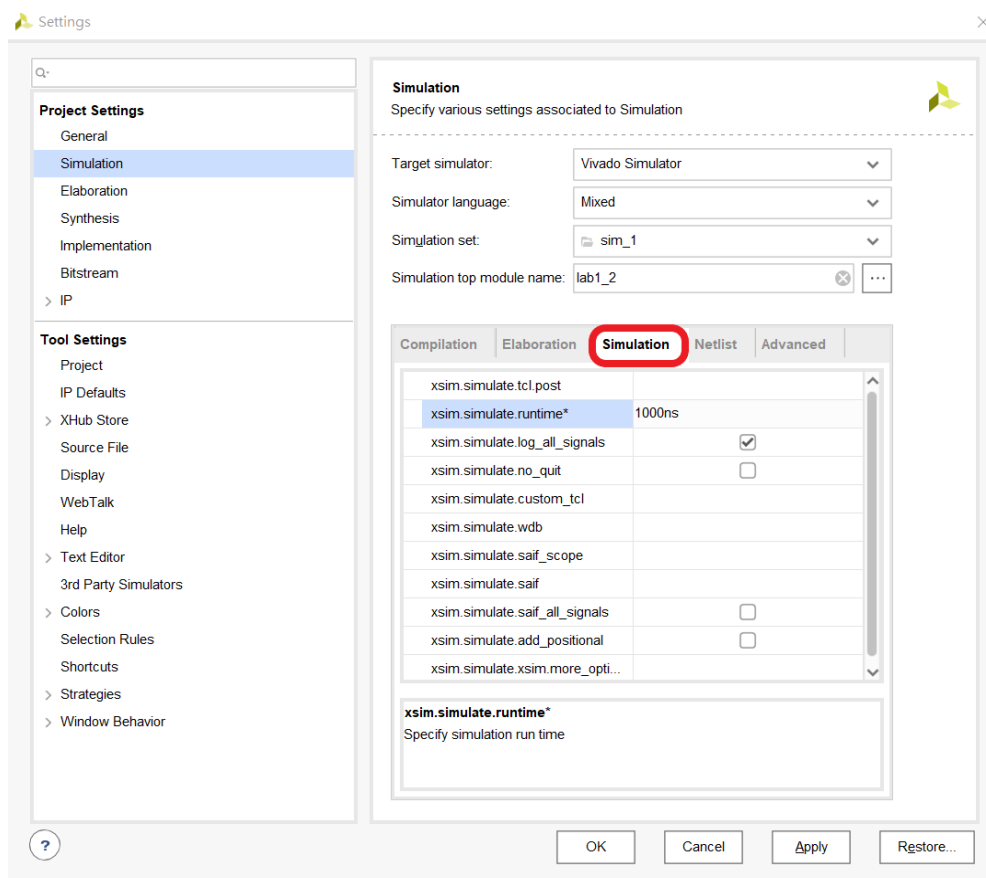

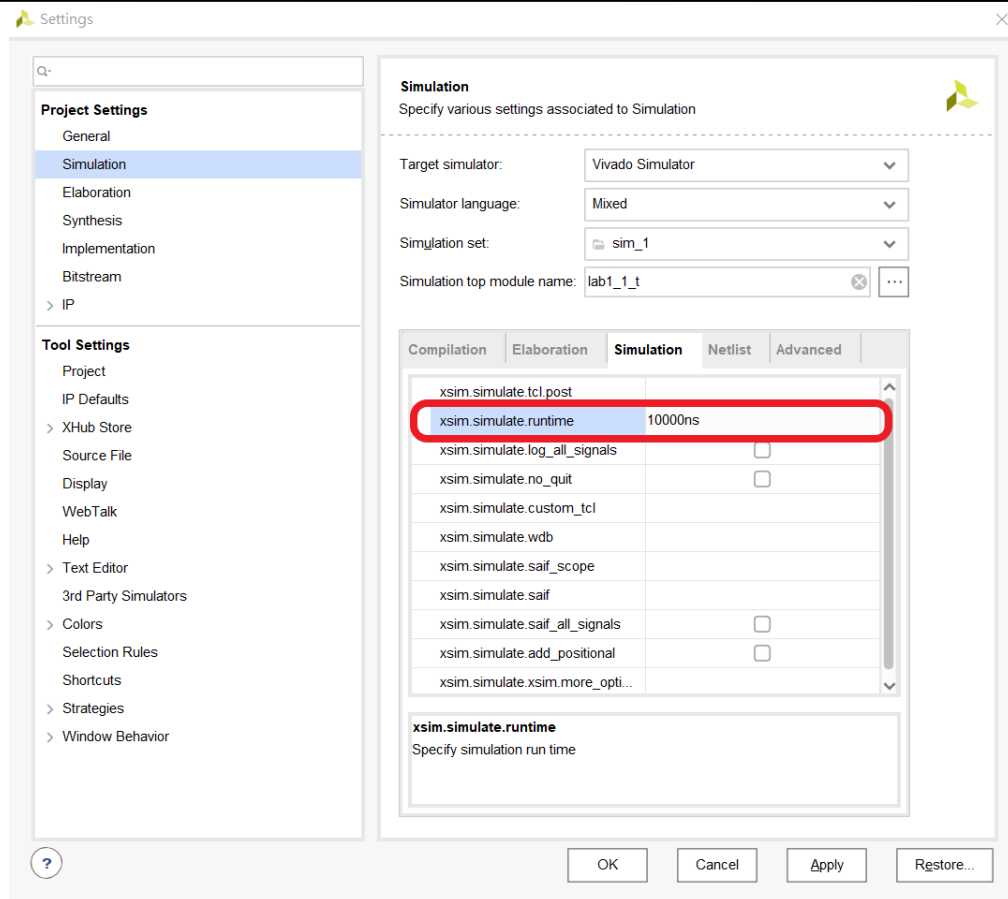3. Change runtime to 10000ns or a larger value.



4. Remember to click Apply.

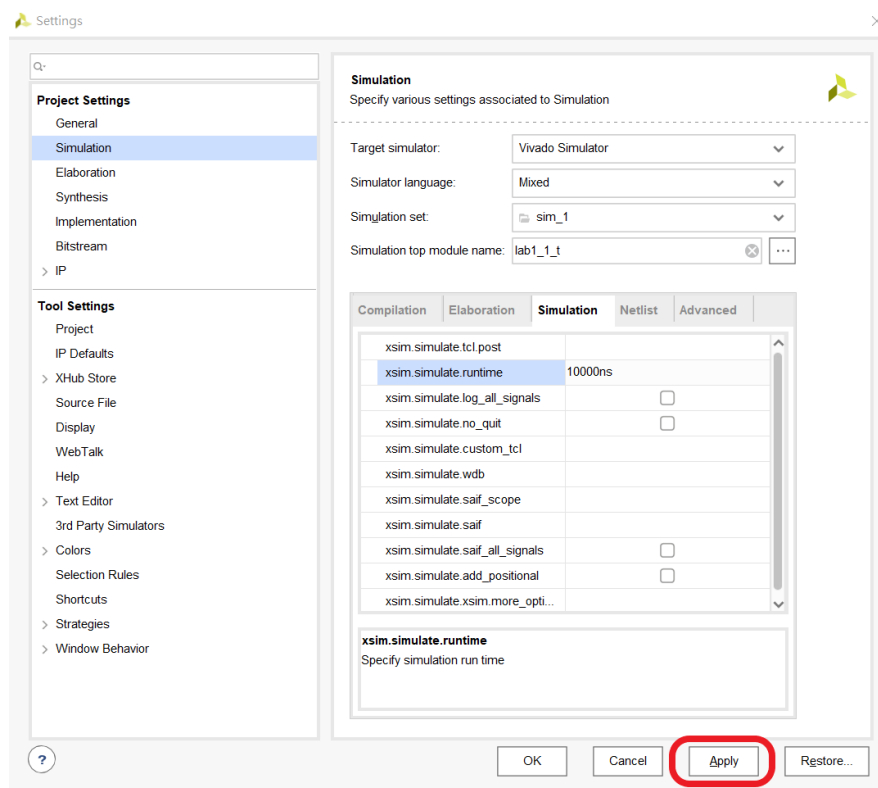

✓ In lab1_2, testing exhausted (all possible) patterns will be time-consuming. So, we provide a public test set of 2^8 patterns with the file of public.dat. Note that we will use

additional hidden test patterns to verify your design.

